

Exercice 1

$$L = 2 \cdot 10^{-7} \ln \frac{GMD}{GMR_L} \quad C = \frac{2\pi\varepsilon}{\ln \left(\frac{GMD}{GMR_C} \right)}$$

$$GMD = \sqrt[3]{D \cdot D \cdot 2D} = \sqrt[3]{2D^3} = 1,26D = 1,26 \times 6 = 7,56m$$

$$GMR_L = \sqrt{GMR \cdot d} = \sqrt{1,148 \times 30} = 5,869 \text{ cm}$$

$$GMR_C = \sqrt{r \cdot d} = \sqrt{1,42 \times 30} = 6,527 \text{ cm}$$

$$L = 2 \cdot 10^{-7} \ln \frac{756}{5,869} = 9,717 \cdot 10^{-7} \text{ H/m} = 0,972 \text{ mH/km}$$

$$C = \frac{2\pi \cdot 8.854 \cdot 10^{-12}}{\ln \left(\frac{756}{6,527} \right)} = 11,71 \cdot 10^{-12} \text{ F/m} = 11,71 \cdot 10^{-9} \text{ F/km}$$

$$R = \left(\frac{R_1}{2} \right) l = \frac{0,08}{2} \times 120 = 4,8 \Omega$$

$$X = (\omega L)l = 314 \times 0,972 \cdot 10^{-3} \times 120 = 36,62 \Omega$$

$$Z = R + jX = 4,8 + j36,62 = 36,93 \angle 82,53^\circ \Omega$$

Exercice 2

$$Z = 12 + j15 = 19,21 \angle 51,34^\circ \Omega$$


1)

$$J = \frac{U}{Z} = \frac{400}{19,21} = 20,82 A$$

$$P = 3RJ^2 = 3 \times 12 \times (20,82)^2 = 15605W \approx 15,61 kW$$

$$Q = 3XJ^2 = 3 \times 15 \times (20,82)^2 = 19506VAr \approx 19,51 kVAr$$
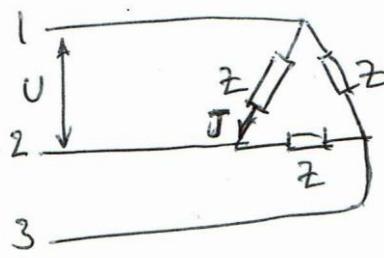
$$S = \sqrt{P^2 + Q^2} = \sqrt{22,18^2 + 14,78^2} = 24,98 kVA$$




2)

$$I = \frac{V}{Z} = \frac{U/\sqrt{3}}{Z} = \frac{400/\sqrt{3}}{19,21} = 12,02 A$$

$$P = 3RI^2 = 3 \times 12 \times (12,02)^2 = 5201W \approx 5,20 kW$$

$$Q = 3XI^2 = 3 \times 15 \times (12,02)^2 = 6502VAr \approx 6,50 kVAr$$
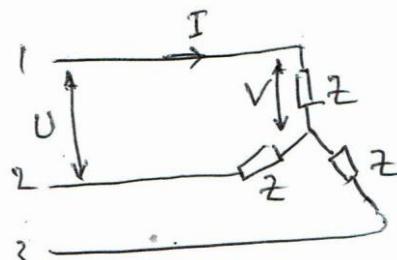
$$S = \sqrt{P^2 + Q^2} = \sqrt{5,20^2 + 6,50^2} = 8,33 kVA$$




3)

$$I_2 = 0$$

$$\bar{I}_N = \bar{I}_1 + \bar{I}_3 = \frac{\bar{V}_1}{Z} + \frac{\bar{V}_3}{Z} = \frac{\bar{V}_1}{Z} + \frac{\bar{V}_1 \angle 120^\circ}{Z}$$

$$\bar{V}_1 = \frac{400}{\sqrt{3}} \angle 0^\circ = 231 \angle 0^\circ V$$

$$\bar{I}_N = \frac{231 + 231 \angle 120^\circ}{19,21 \angle 51,34^\circ} = 12,02 \angle 8,66^\circ A$$

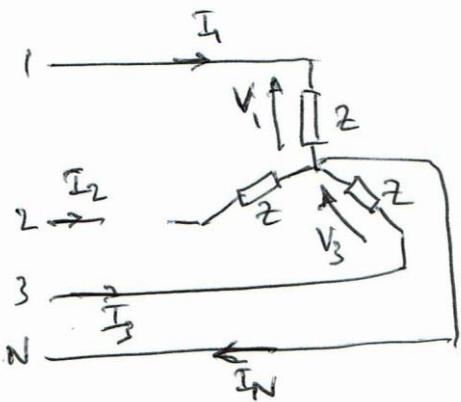

Exercice 3

$$\bar{U}_S = 360 \angle 10^\circ kV \quad \bar{U}_R = 375 \angle 0^\circ kV$$

$$\bar{I} = \frac{\bar{V}_S - \bar{V}_R}{Z} = \frac{\bar{U}_S - \bar{U}_R}{\sqrt{3} \cdot Z} = \frac{360 \angle 10^\circ - 375 \angle 0^\circ}{\sqrt{3} \cdot (4 + j32)} = 1177,6 \angle 25,26^\circ A$$

$$\bar{S}_S = \sqrt{3} \cdot \bar{U}_S \cdot \bar{I}^* = \sqrt{3} \cdot 360 \angle 10^\circ \cdot (1,1776 \angle 25,26^\circ)^* = 734,28 \angle -15,26^\circ MVA$$

$$\rightarrow P_S = 708,39 MW \quad Q_S = -193,26 MVar$$

$$\bar{S}_R = \sqrt{3} \cdot \bar{U}_R \cdot \bar{I}^* = \sqrt{3} \cdot 375 \angle 0^\circ \cdot (1,1776 \angle 25,26^\circ)^* = 764,87 \angle -25,26^\circ MVA$$

$$\rightarrow P_R = 691,74 MW \quad Q_S = -326,39 MVar$$

$$\Delta P = P_S - P_R = 708,39 - 691,74 = 16,65 MW$$