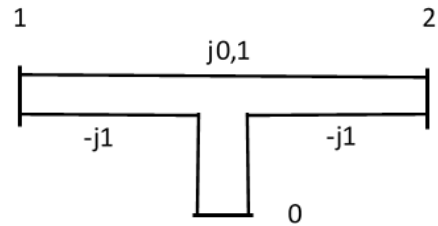


## CALCULATION OF ELECTRICAL NETWORK MATRICES

### Exercise 1

Consider the following network.

- 1) Find the admittance matrix  $Y$ .
- 2) Form the impedance matrix  $Z$  following the order 0-1, 1-2, and 0-2.



### Exercise 2

Let  $Y$  be the admittance matrix of a 3-bus network.

$$Y = \begin{bmatrix} 35 & -10 & -20 \\ a & 25 & 0 \\ -20 & b & c \end{bmatrix}$$

- 1) Find  $a$  and  $b$ .
- 2) Given that bus 3 is not connected to the reference bus, find  $c$ .

### Exercise 3


Let  $Y$  be the admittance matrix of a 3-bus network.

$$Y = \begin{bmatrix} a & -5 & -10 \\ -5 & 20 & -15 \\ -10 & -15 & 25 \end{bmatrix}$$

Bus 2 is to be eliminated, find the value of  $a$  if  $Y_{11}$  becomes equal to 33.25.
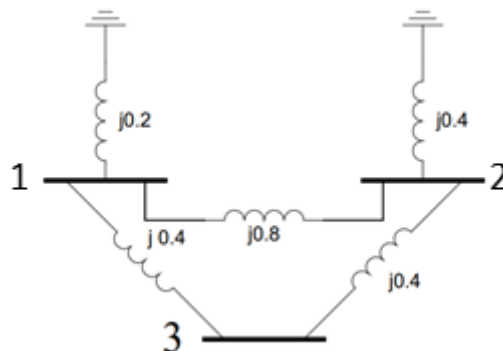
### Exercise 4

Consider the 3-bus electrical network in the figure below.



- 1) Form the matrix  $Y_{bus}$
- 2) Construct the  $Z_{bus}$  matrix by following the order of the following elements: 1-0, 2-0, 1-3, 1-2 and 2-3.

**Reminder:  $Z_{bus}$  construction formulas**

**Table 4.1 Summary of equations for formation of bus impedance matrix**

Add P-Q	Mutual coupling		No mutual coupling	
	p is not the reference bus	p is the reference bus	p is not the reference bus	p is the reference bus
<b>Branch</b>	$Z_{qi} = Z_{pi} + \frac{\bar{y}_{pq,ps}(\bar{Z}_{pi} - \bar{Z}_{si})}{y_{pq,ps}}$ $i = 1, 2, \dots, m$ $i \neq q$ $Z_{qq} = Z_{pq} + \frac{1 + \bar{y}_{pq,ps}(\bar{Z}_{pq} - \bar{Z}_{sq})}{y_{pq,ps}}$	$Z_{qi} = \frac{\bar{y}_{pq,ps}(\bar{Z}_{pi} - \bar{Z}_{si})}{y_{pq,ps}}$ $i = 1, 2, \dots, m$ $i \neq q$ $Z_{qq} = \frac{1 + \bar{y}_{pq,ps}(\bar{Z}_{pq} - \bar{Z}_{sq})}{y_{pq,ps}}$	$Z_{qi} = Z_{pi}$ $i = 1, 2, \dots, m$ $i \neq q$ $Z_{qq} = Z_{pq} + z_{pq,ps}$	$Z_{qi} = 0$ $i = 1, 2, \dots, m$ $i \neq q$ $Z_{qq} = z_{pq,ps}$
<b>Link</b>	$Z_{li} = Z_{pi} - Z_{qi} + \frac{\bar{y}_{pq,ps}(\bar{Z}_{pi} - \bar{Z}_{si})}{y_{pq,ps}}$ $i = 1, 2, \dots, m$ $i \neq l$ $Z_{ll} = Z_{pl} - Z_{ql} + \frac{1 + \bar{y}_{pq,ps}(\bar{Z}_{pl} - \bar{Z}_{sl})}{y_{pq,ps}}$	$Z_{li} = -Z_{qi} + \frac{\bar{y}_{pq,ps}(\bar{Z}_{pi} - \bar{Z}_{si})}{y_{pq,ps}}$ $i = 1, 2, \dots, m$ $i \neq l$ $Z_{ll} = -Z_{ql} + \frac{1 + \bar{y}_{pq,ps}(\bar{Z}_{pl} - \bar{Z}_{sl})}{y_{pq,ps}}$	$Z_{li} = Z_{pi} - Z_{qi}$ $i = 1, 2, \dots, m$ $i \neq l$ $Z_{ll} = Z_{pl} - Z_{ql} + z_{pq,ps}$	$Z_{li} = -Z_{qi}$ $i = 1, 2, \dots, m$ $i \neq l$ $Z_{ll} = -Z_{ql} + z_{pq,ps}$
Modification of the elements for elimination of lth node				
$Z_{ij} \text{ (modified)} = Z_{ij} \text{ (before elimination)} - \frac{Z_{il}Z_{lj}}{Z_{ll}} \quad i, j = 1, 2, \dots, m$				